 


Lecture 12

Latches



- RS Latch

- A cross is used in 2 symmetric NOR switches such that the output of one NOR gate is used as the input of the other NOR gate, and the second input is either R or S.
- R stands for reset, and S stands for set. If we change the voltages (**in bold**),

R	S	Q	\bar{Q}
1	0	0	1
0	$0 \rightarrow 1$	$0 \rightarrow 1$	$1 \rightarrow 0$
0	0	1	0
1	0	0	1
1	1	0	0
0	0	oscillates	oscillates

- Gated RS Latch

- A clock is added to disable and enable the latch
 - A clock is square wave generated by a crystal oscillator
- | Clock | S | R | Q(t+1) |
|-------|-----|-----|----------|
| 0 | Any | Any | Q(t) |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | not used |

This circuit is built by replacing R and S with R' and S' respectively, where R' = clock AND R, and S' = clock AND S.

If we let $R = D$ and $S = \sim D$, we have

Clock	D	$Q(t+1)$
0	Any	$Q(t)$
1	0	0
1	1	1

D is the data input, where when clock = 1, $Q = D$, but when clock = 0, Q stores the present value of D. Any circuit with this truth table is a gated D latch.

Flip Flops

- Clock = 0: $Q_m=0$, Q = stored value
- Clock = 1: $Q = Q_m = D$ (no longer racks input changes)
- Summary: when clock changes from 0 to 1, the value of D **at that moment** is stored in FF